 



<u>Lab Manual # 08</u> <u>Combinational Circuits using System Verilog</u>


<u>Name</u>	<u>Muddassir Ali Siddiqui</u>
Instructor	Sir Musaddiq Hussain & Sir Bilal
<u>Date</u>	<u> 30th July 2025</u>


1. In-Lab Tasks: (Write your lab task & screenshots here)


i. Task 1:



 


 


 


 


ii. Task 2:

 


 


 


iii. Task 3:

 


 


 

 



iv. Task 4:

 

 

v. Task 5:

 

 

2. FPGA Outputs:

Task 1:





Task 2:



Task 3:



Task 4:



3. Critical Analysis: (Write you critical analysis / conclusion here)

In this lab we design in task 1 mux with 3 different approaches by gate level, case statement and behavioral. In task 2 we convert BCD to seven segment and show output on the FPGA's 7-segment display. In task 3 we perform priority encoder by analyzing the truth table. In task 4 we do barrel shifter left and right by giving the direction to shift. In task 5 carry lookahead adder is performed by me.