



NUST CHIP DESIGN CENTRE


Digital Logic Design

DLD Task: 4-bit ALU


<u>Name</u>	<i><u>Muddassir Ali Siddiqui</u></i>
<u>Instructor</u>	<i><u>Sir Musaddiq Hussain & Sir Bilal</u></i>
<u>Date</u>	<i><u>30th July 2025</u></i>

1. In-Lab Tasks: (Write your lab task & screenshots here)


Schematic:

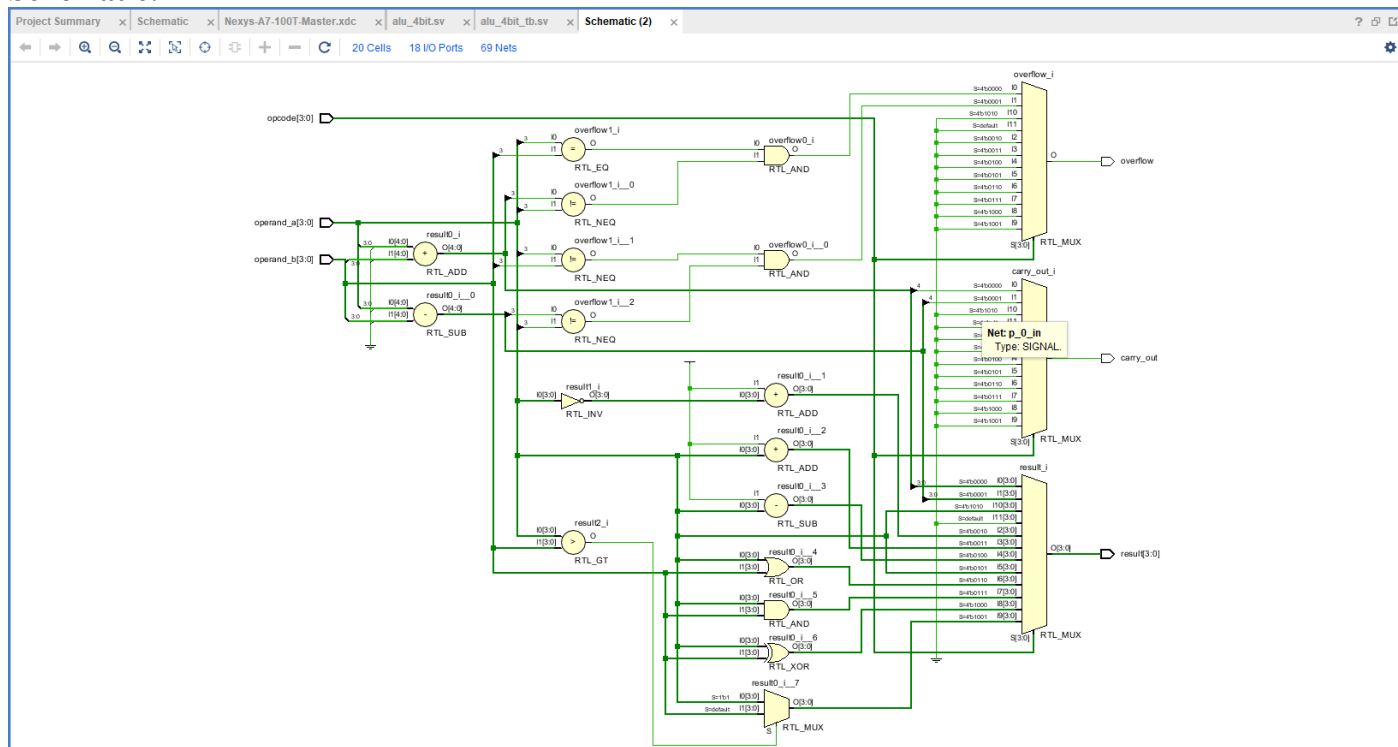


Bitstream Generation Popup:

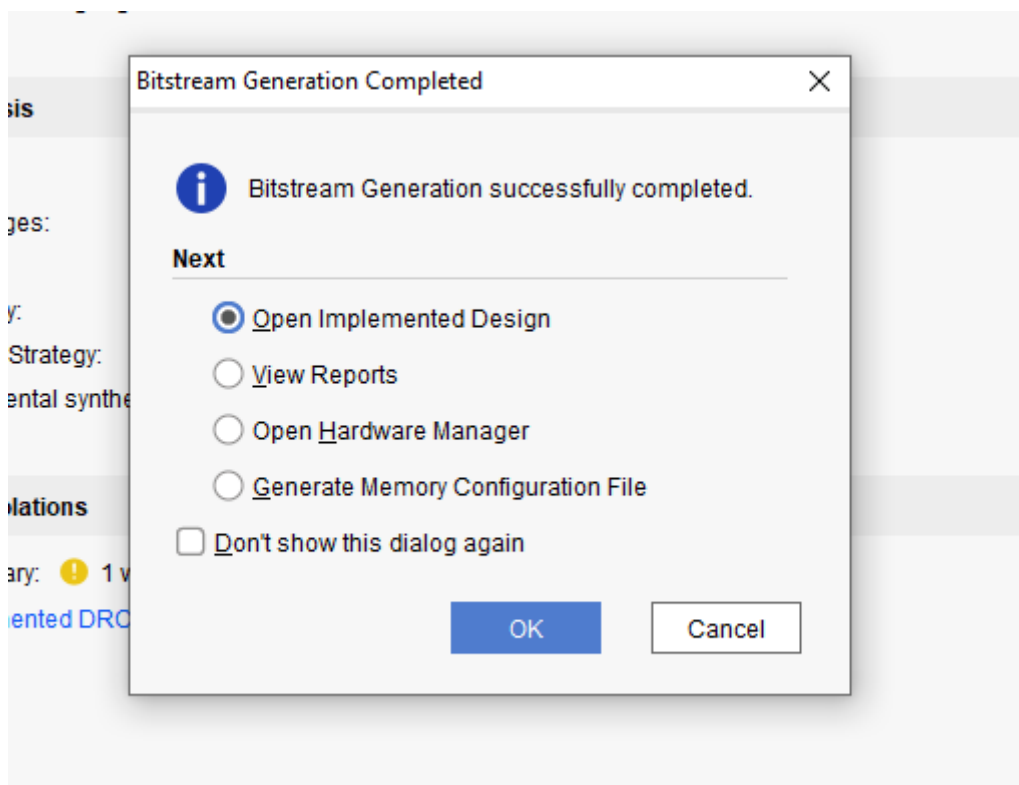

Area, Timing, and Power Reports:

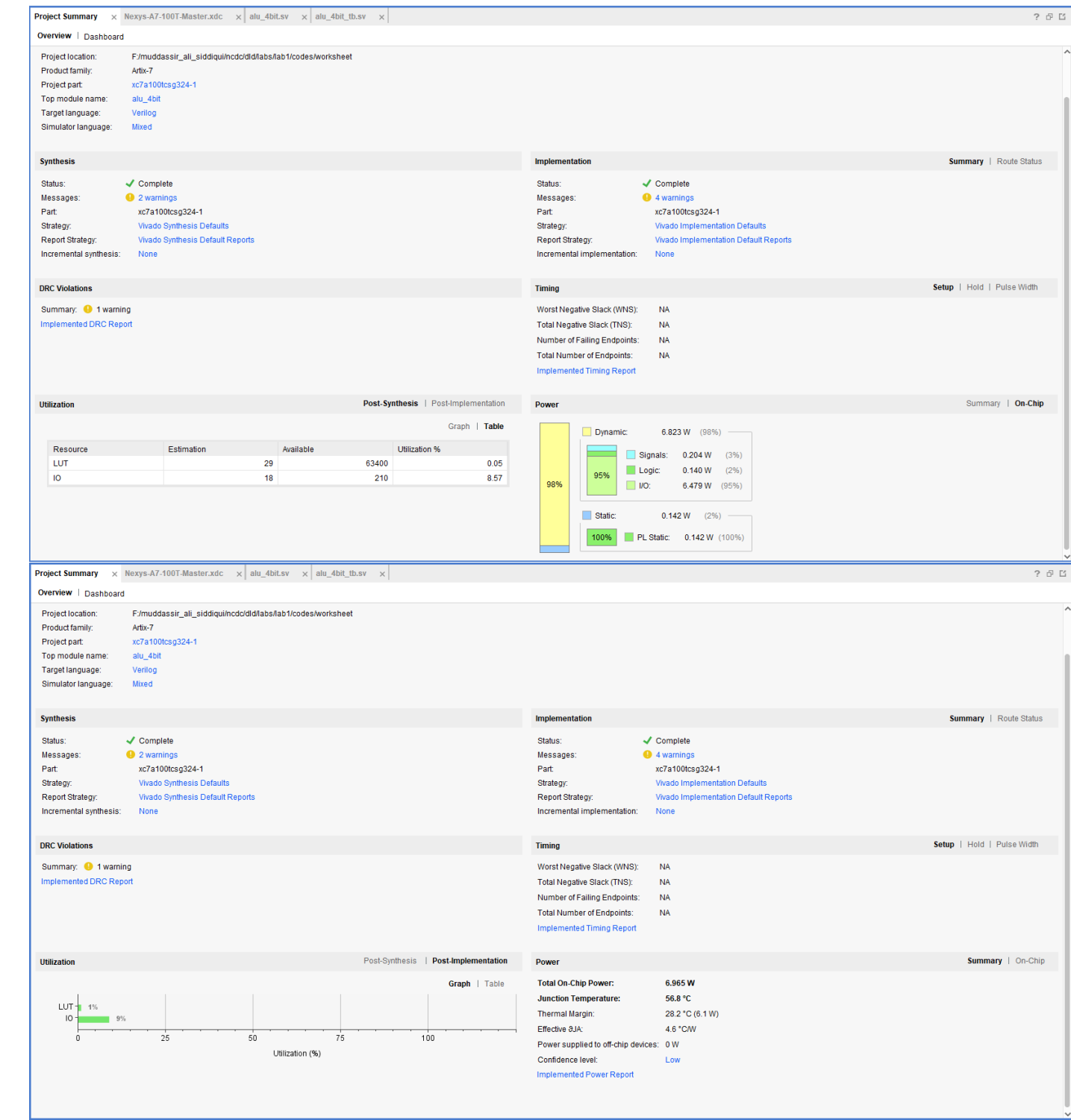

Waveform:

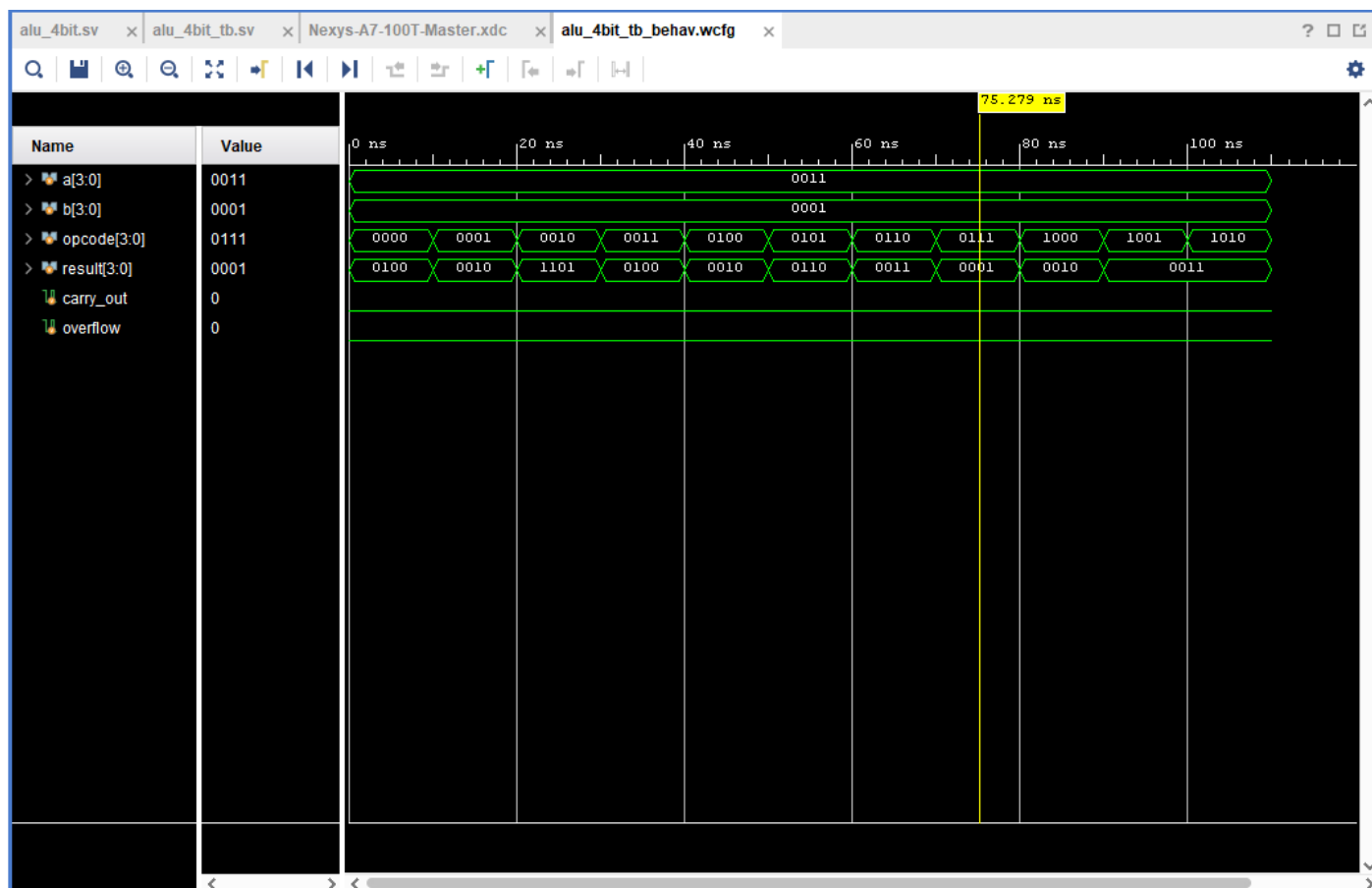

In the above waveform we assign operand_a = 0011 and operand_b = 0001, and result store the result of the operations.

2. Critical Analysis: (*Write you critical analysis / conclusion here*)

In this task we design a 4-bit alu in which we assign 10 operations given in the manual by mux. The alu is the critical and important section of a processor.